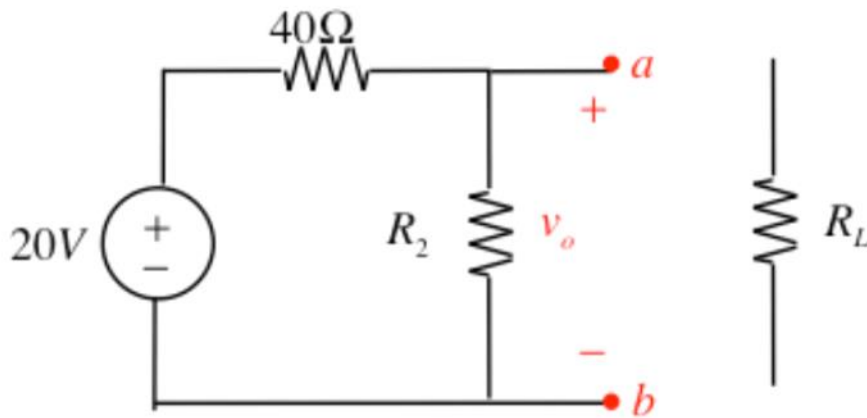


Exercise 3, Question 1

(discussion problem 2, Question 2)


In the voltage-divider circuit shown, the no-load value of v_0 is 4v. When the load resistance R_L is attached across the terminals a and b , v_0 drops to 3v.

- Find the value of R_2
- Find the value of R_L




Exercise 3, Question 2

Use Superposition to find i_1 and i_2 .

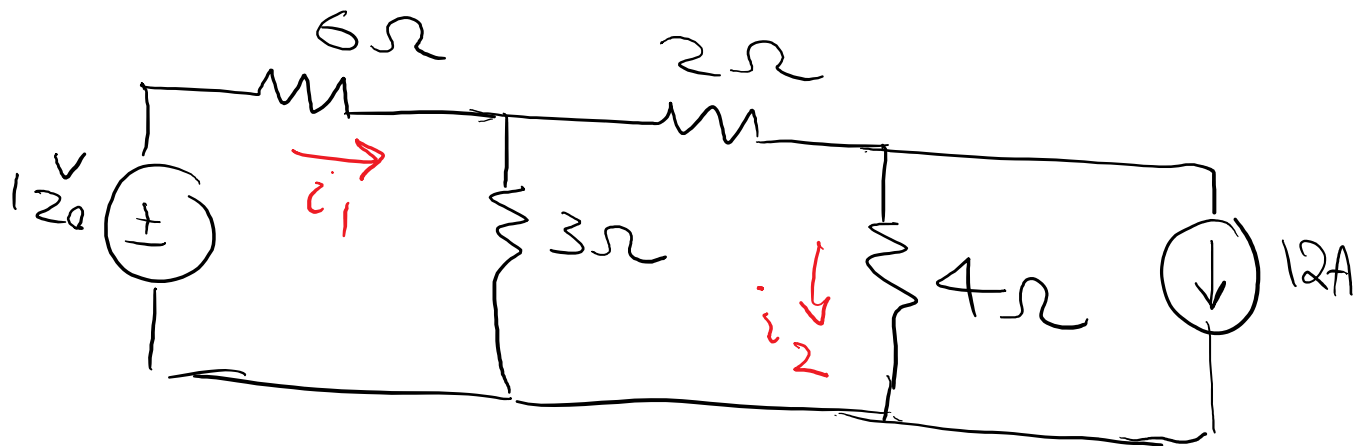



Exercise 3, Question 3a

Find Req

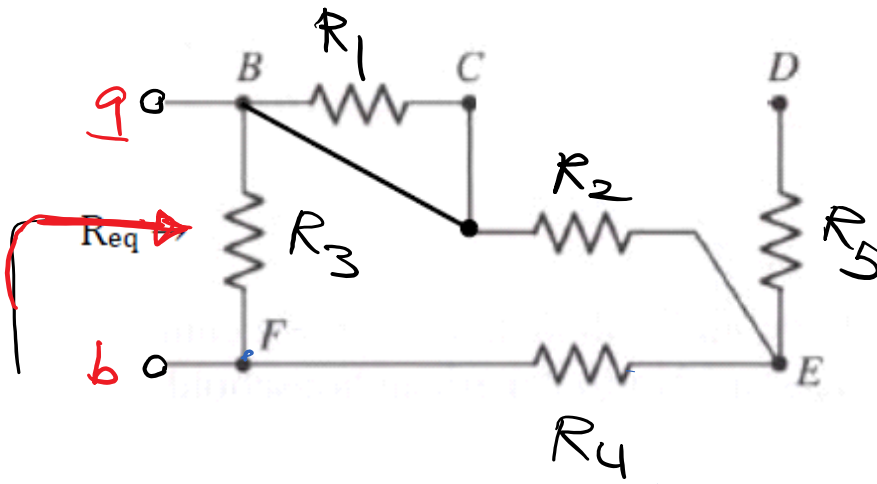

Exercise 3, Question 3b, 3c

Find R_{eq} seen from terminals a and b.

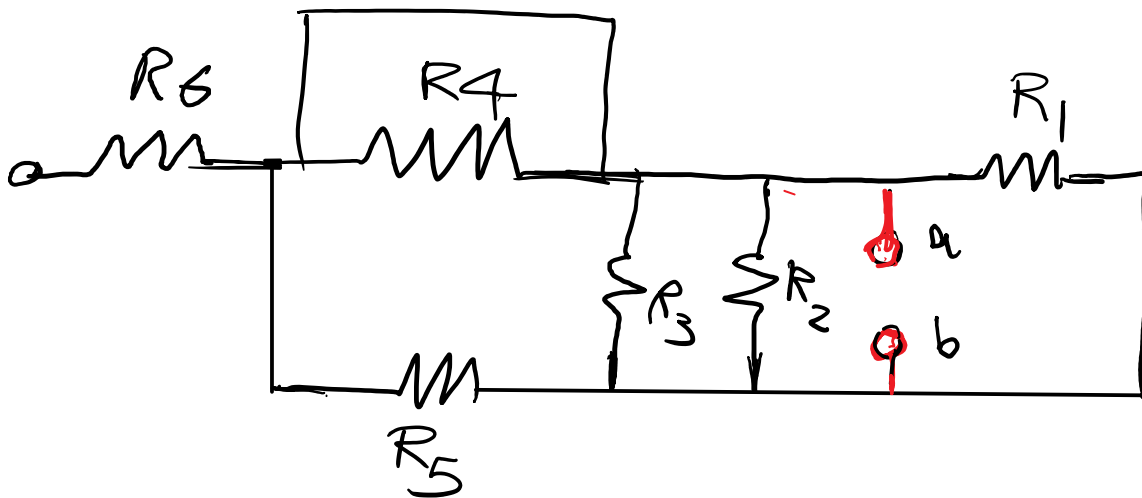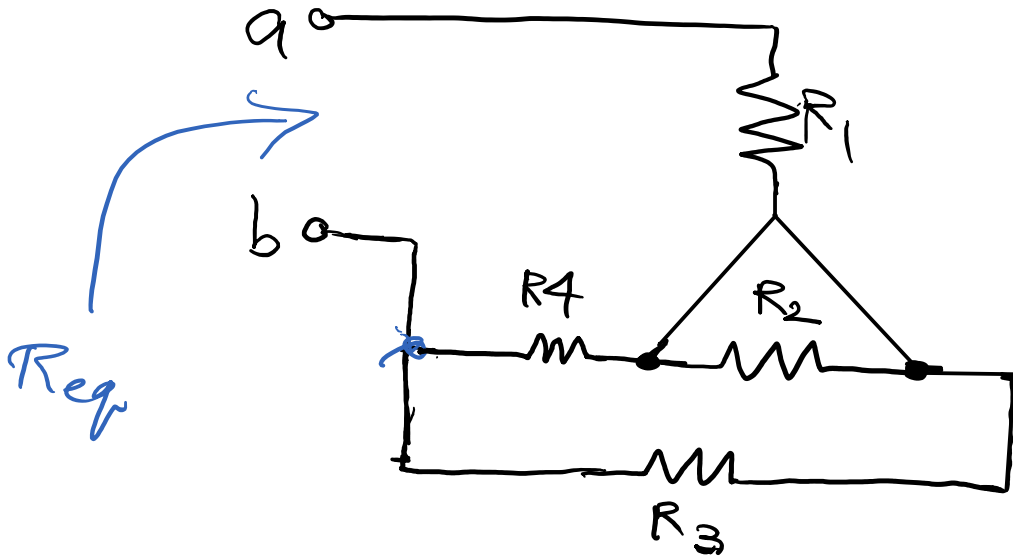

Exercise 3, Question 4

- a) Use Kirchhoff's laws and Ohm's law to find the voltage v_o as shown in Fig. 2.23.
- b) Show that your solution is consistent with the constraint that the total power developed in the circuit equals the total power dissipated.

